



Name: SUBHOJIT GHIMIRE
Roll No.: 1912160
Section: C.S.E. 'K'

ELECTRICAL ASSIGNMENT - I

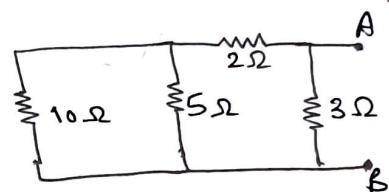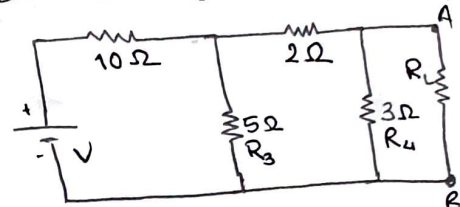Q.1. Calculate the value of R_L at which maximum power transfer takes place. Calculate the maximum power.

Soln: To find R_{th} ,

$$R_{th} = \frac{\left(\frac{10}{3} + 2\right) \times 3}{\left(\frac{10}{3} + 2\right) + 3} = 1.92 \Omega$$




we know, for P_{max} ,

$$R_L = R_{th} = 1.92 \Omega$$

Now,
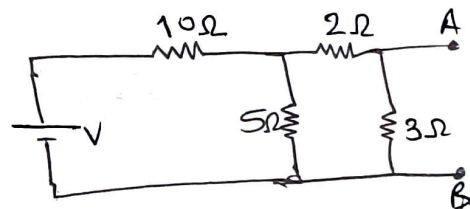
$$R_{eq} = \frac{5}{2} + 10 = 12.5 \Omega$$



$$\text{Total Current in circuit,} = \frac{V}{12.5} \text{ A}$$



$$\text{Current through } 3 \Omega = \frac{V}{12.5 \times 2} = \frac{V}{25} \text{ A}$$

$$\therefore V_{3\Omega} = \frac{3}{25} V = 0.12 V$$

2. Find the currents I_1 , I_2 , I_3 and powers delivered by the sources of the network shown below:

Soln:-

Remaking the circuit,

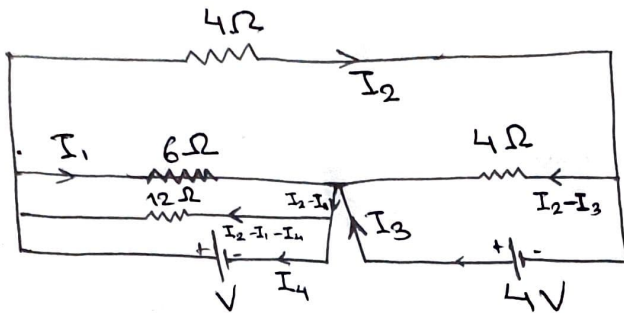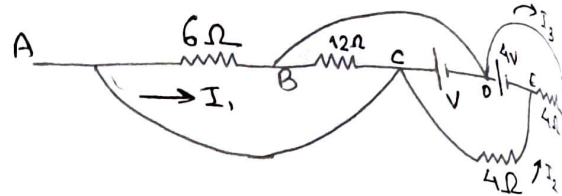

Using mesh analysis,

$$(i) \quad 4I_2 + 4(I_2 - I_3) - 6I_1 = 0$$

$$\therefore 6I_1 - 8I_2 + 4I_3 = 0 \quad \text{--- (i)}$$

$$(ii) \quad 4(I_2 - I_3) = -4V,$$

$$\therefore 4I_2 - 4I_3 = -4V \quad \text{--- (ii)}$$

$$(iii) \quad 6I_1 + 12(I_2 - I_1 - I_4) = 0$$

$$\therefore 6I_1 - 12I_2 + 12I_4 = 0 \quad \text{--- (iii)}$$

$$(iv) \quad 12(I_2 - I_1 - I_4) = -1V$$

$$\therefore +12I_1 - 12I_2 + 12I_4 = 1V \quad \text{--- (iv)}$$

This gives,

$$I_1 = 1V \text{ A}$$

$$I_2 = 1.25V \text{ A}$$

$$I_3 = 2.25V \text{ A}$$

for, $V = 60V$,

$$I_1 = 6V, \quad I_2 = 75A, \quad I_3 = 135A$$

1912160

∴ Power from Source Supplies,

$$\begin{aligned} \text{Power delivered by } V &= \frac{3}{2} \times V^2 = \frac{3}{2} \times (60)^2 \\ &= 5400 \text{ W} \\ &= 5.4 \text{ kW} \end{aligned}$$

$$\begin{aligned} \text{Power delivered by } 4V &= 4V I_3 \\ &= 4 \times 60 \times 135 \\ &= 32400 \text{ W} \\ &= 32.4 \text{ kW} \end{aligned}$$



3. Find the current through 10Ω resistor using Thevenin's theorem for the given circuit:

Soln: for R_{th}

$$R_{th} = \frac{(5+R) \times 1}{5+R+1}$$


for $R = 60\Omega$,

$$R_{th} = 0.984\Omega$$

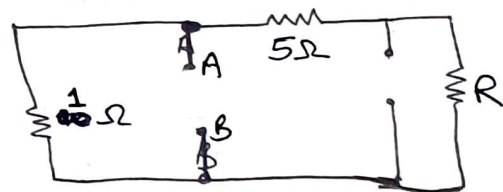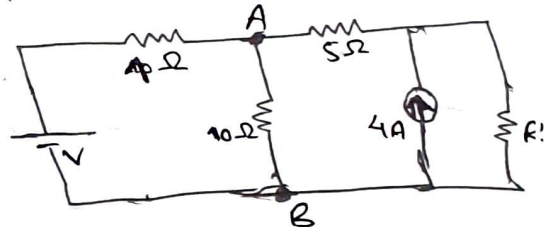

for V_{th}
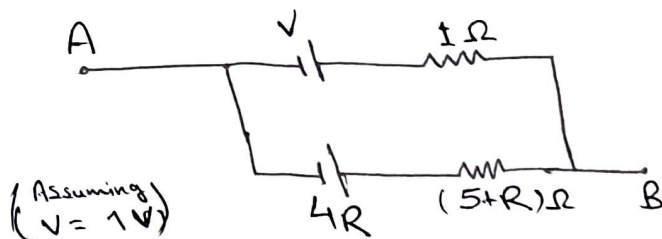
$$\begin{aligned} V_{th} &= \frac{\frac{1V}{1} + \frac{4 \times 60}{5+60}}{1 + \frac{1}{5+60}} \\ &= \frac{1 + \frac{240}{65}}{1 + \frac{1}{65}} \end{aligned}$$



(Assuming $V = 1V$)

$$\therefore V_{th} = 4.62 \text{ V}$$

1912160

Making Thevenin's Equivalent Circuit,

Current through 10Ω ,

$$= \frac{V_{th}}{10 + R_{th}}$$

$$= \frac{4.62}{10 + 0.984}$$

$$\therefore I = 0.420 \text{ A}$$

(Taking $V = 1\text{V}$
Taking $R = 60\Omega$)





4. Obtain value of R_L and P_{max} through maximum power transform theorem for given circuit.

Soln: for R_{th} ,

$$R_{th} = \frac{(20 + 10) \times 30}{20 + 10 + 30}$$

$$\therefore R_{th} = 15\Omega$$

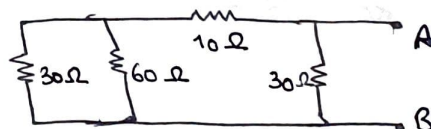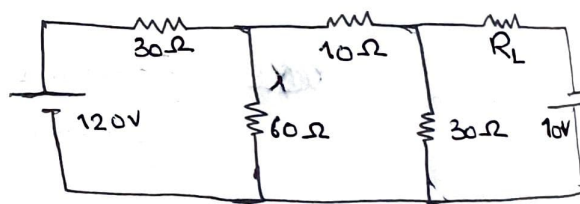

In max power theorem,

$$R_L = R_{th} = 15\Omega$$


Now,

$$R_{eq} = 30 + \frac{60(30 + 10)}{60 + 30 + 10}$$

$$\therefore R_{eq} = 54\Omega$$

$$\therefore \text{Total current in circuit} = \frac{120}{54} = 2.22 \text{ A}$$
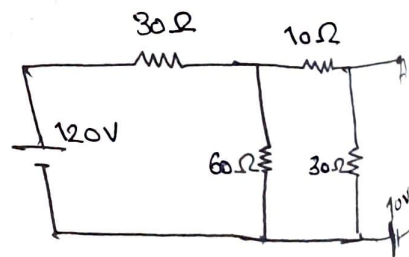
$$\text{Current through } 10\Omega \text{ resistor} = \frac{20}{3} \times \frac{60}{60 + 40} = 1.33 \text{ A}$$



for V_{th} ,


Here, $V_{80\Omega} = 30 \times \frac{4}{3} = 40V$

$$V_A - 10V = 40V$$

$$\therefore V_A = 50V$$

$$V_{AB} = 50 - 0 = 50V$$

$$\therefore V_{th} = V_{AB} = 50V$$

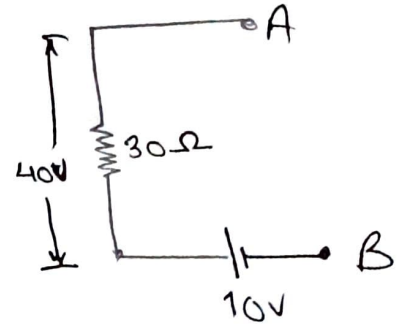

$$\text{So, } P_{max} = \frac{V_{th}^2}{4R_L} = \frac{2500}{4 \times 15} = 41.67 W$$



5. Find the current through 20Ω resistor using thevenin's theorem for the circuit :

Soln: for R_{th} ,

$$R_{th} = \frac{30 \times (R + 10)}{30 + R + 10}$$


for $R = 60\Omega$

$$R_{th} = 21\Omega$$

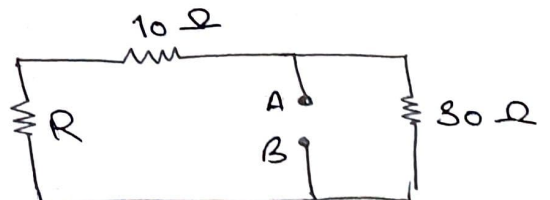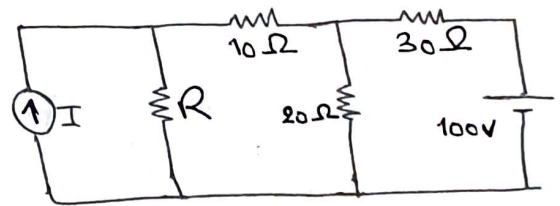

for V_{th} ,
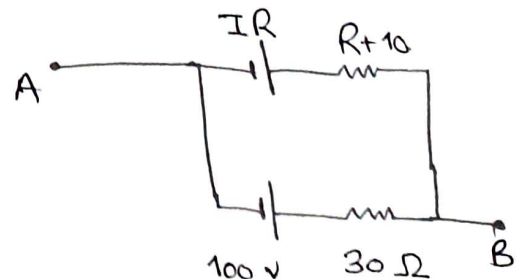
$$V_{th} = \frac{\frac{100}{30} + \frac{IR}{R+10}}{\frac{1}{30} + \frac{1}{R+10}}$$



for $I = R = 60$,

$$V_{th} = 1150V$$

1912160


Making Thevenin's Eqv. Circuit,

Current through 20Ω ,

$$= \frac{V_{th}}{20 + R_{th}}$$




$$= \frac{1150}{20 + 21}$$

$$\therefore I = 28.04 \text{ A}$$

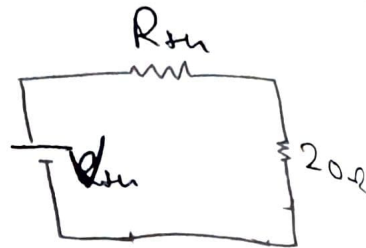

6. Verify the reciprocity theorem (for I_2') in the given circuit,

Soln:- CASE I:

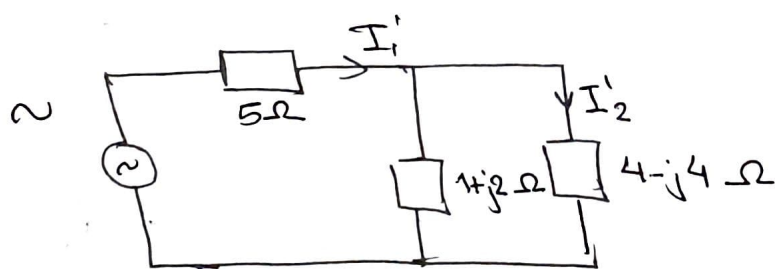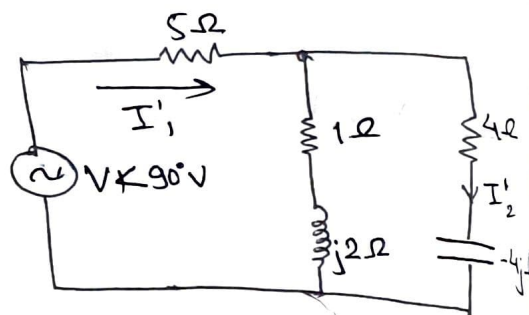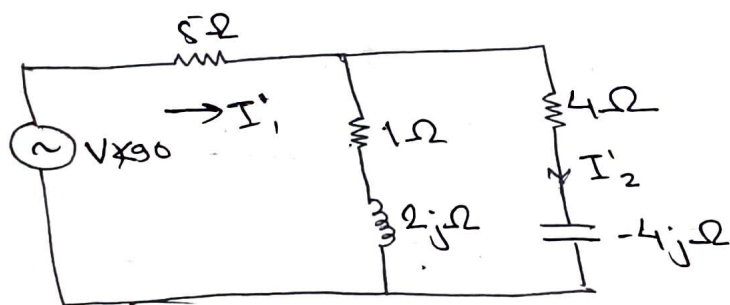

$$Z_{eq} = \frac{5 + (1 + j2)(4 - j4)}{5 - j2} = 6.96 \angle 12.59^\circ \Omega$$


$$\text{So, } I_1' = \frac{V \angle 90^\circ}{6.96 \angle 12.59^\circ}$$

for $V = 60 \text{ V}$,


$$I_1' = 8.62 \angle 77.41^\circ \text{ A}$$

$$\text{And, } I_2' = I_1' \times \frac{(1 + j2)}{5 - j2} = 3.5773 \angle 162.64^\circ \text{ A}$$

CASE II :

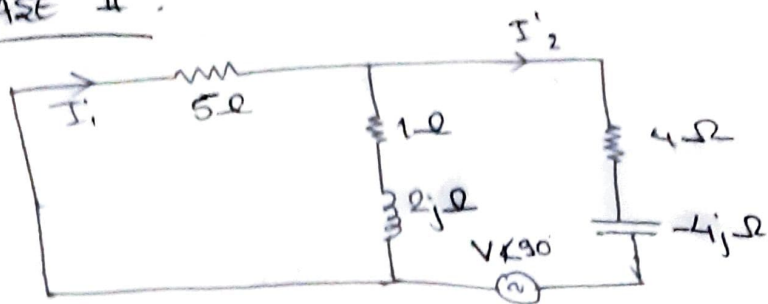

\Rightarrow

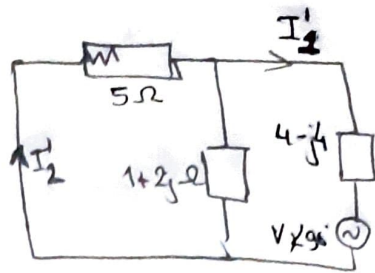

$$Z_{eq} = 4 - j4 + \frac{5(1 + j2)}{6 + j2} = 5.934 - j27.64 \Omega$$

So,

$$I'_1 = \frac{V \angle 90^\circ}{5.934 - j27.64^\circ}$$

for $V = 60V$,

$$I'_1 = 10.118 \angle 117.64^\circ \text{ A}$$

$$\text{And, } I'_2 = I'_1 \times \frac{(1 + j2)}{6 + j2}$$

$$\therefore I'_2 = 3.571 \angle 162.64^\circ \text{ A}$$

Since, I'_2 in case I $= I'_2$ in case II

hence,

\therefore Reciprocity Theorem has been proved.

7. An inductor draws 5 A when connected to 100V, 50 Hz supply. The resistance of the coil is 5Ω . Determine
- (i) Inductance
 - (ii) Real Power, Reactive Power
 - (iii) Apparent Power.

Soln:-

Given,

$$f = 50 \text{ Hz} \rightarrow \omega = 2\pi f = 314 \text{ rad/s}$$

$$I = 5 \text{ A}$$

$$V = 100 \text{ V}$$

$$\therefore Z = \frac{100}{5} = 20 \Omega$$

$$R = 5 \Omega$$

(i) So,

$$X_L = \omega L = 314L$$

$$Z^2 = \sqrt{R^2 + X_L^2}$$

$$\therefore 20^2 = \sqrt{5^2 + (314L)^2}$$

$$\therefore 400 = \sqrt{25 + 98596L^2}$$

$$\therefore 400 = 25 + 98596L^2$$

$$\therefore L = \sqrt{\frac{375}{98596}} = 0.0616 \text{ H}$$

$$\therefore \text{Inductance} = 62 \text{ mH}$$

$$(ii) \cos \theta = \frac{R}{Z} = \frac{5}{20} = \frac{1}{4} = 0.25$$

$$\therefore \text{Real Power} = VI \cos \theta = 100 \times 5 \times 0.25 = 125 \text{ W}$$

$$\therefore \text{Reactive Power} = VI \sin \theta = 100 \times 5 \times \sqrt{1 - (0.25)^2} = 484.12 \text{ VAr}$$

$$(iii) \therefore \text{Apparent Power} = VI = 100 \times 5 = 500 \text{ VA}$$

8. A series RC circuit has resistance of 50Ω , and capacitance of $1000\mu\text{F}$ connected in series across a single phase 230V , 50Hz supply. Calculate
- current drawn by circuit
 - Power factor of the circuit
 - Active and reactive power consumed by circuit.
- Draw the phasor diagram.

Soln

Given, $f = 50\text{Hz} \rightarrow \omega = 2\pi f = 314 \text{ rad/s}$

$$R = 50\Omega$$

$$C = 1000\mu\text{F} = 10^{-3}\text{F}$$

$$\text{So, } X_C = \frac{1}{\omega C} = 3.185\Omega$$

$$V = 230\text{V}$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{50^2 + (3.185)^2} = 50.101\Omega$$


$$(i) \text{ So, Current, } I = \frac{V}{Z} = \frac{230}{50.101} = 4.59\text{A}$$

$$(ii) \text{ Power factor, } \cos\theta = \frac{R}{Z} = \frac{50}{50.101} = 0.997$$

$$(iii) \therefore \text{ Active power} = VI\cos\theta = 230 \times 4.59 \times 0.997 = 1052.53\text{W}$$

$$\therefore \text{ Reactive Power} = VI\sin\theta = 230 \times 4.59 \times \sqrt{1 - (0.997)^2} = 81.71\text{VAR}$$

(iv) Phasor diagram

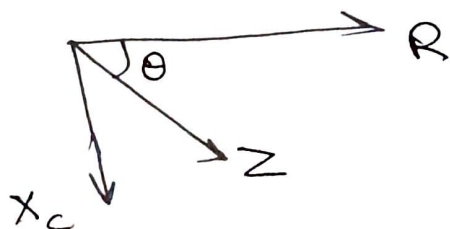


Power Triangle




[1912160]

Q. Prove that, the total power measured in a three phase system using two wattmeter method is $\sqrt{3} V_L I_L \cos \theta$ with relevant phasor diagrams.

Soln Circuit Diagram:

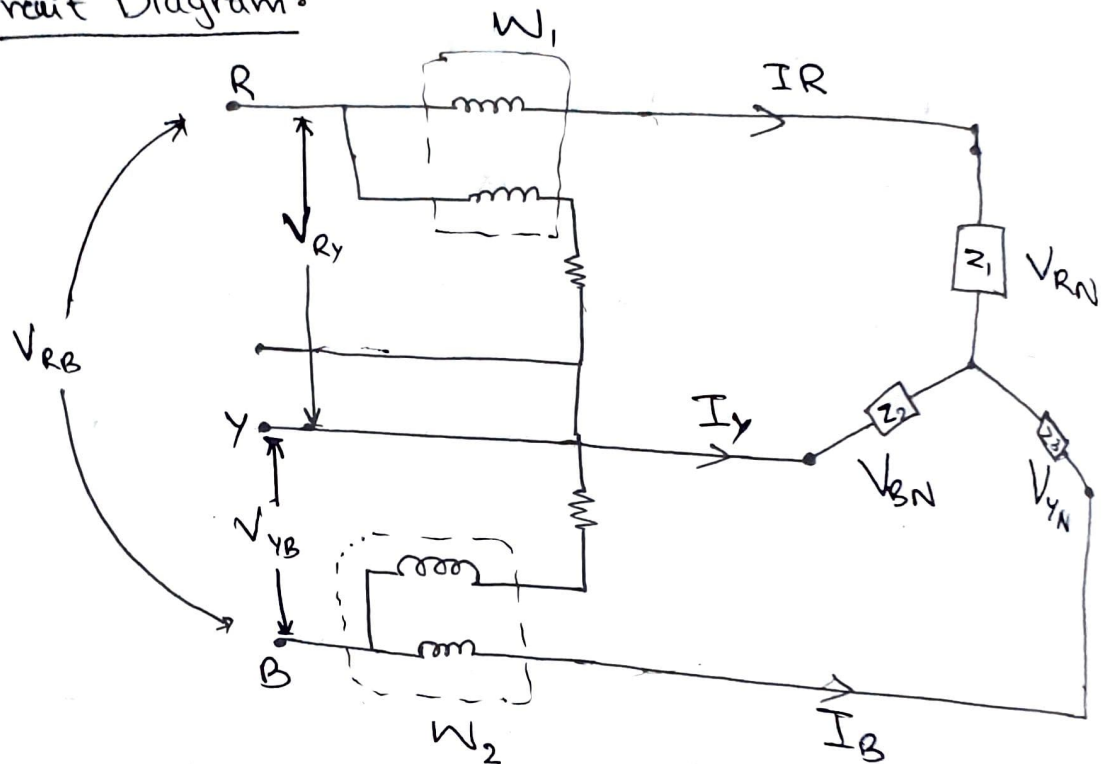

Phasor Diagram:

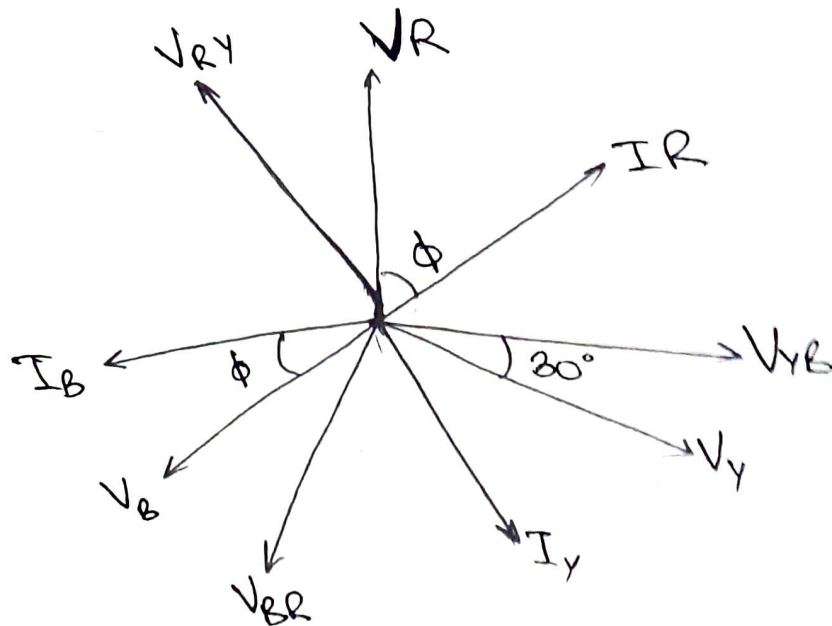

Total Power of the system is:

$$W = I_R \cdot V_{RN} + I_Y \cdot V_{YN} + I_B \cdot V_{BN}$$

Also, the sum of two wattmeters is,

$$W_1 + W_2 = I_R \cdot V_{RN} + I_Y \cdot V_{YN} + I_B \cdot V_{BN}$$

$$\Rightarrow W = W_1 + W_2$$

Now, I_{Ph} lags behind V_{Ph} by $\phi = \phi_p$

Power of two wattmeters.

$$\begin{aligned} \therefore W_1 &= V_{RY} I_R \cos \theta \\ &= V_{RY} I_R \cos (30^\circ + \phi) \\ &= \sqrt{3} V_{Ph} I_{Ph} \cos (30^\circ + \phi) \end{aligned}$$

$$\begin{aligned} \text{and, } W_2 &= V_{BY} I_B \cos \theta \\ &= \sqrt{3} V_{Ph} I_{Ph} \cos (30^\circ - \phi) \end{aligned}$$



$$\begin{aligned} \therefore \text{Total Power, } W &= W_1 + W_2 \\ &= \sqrt{3} V_{Ph} I_{Ph} [\cos (30^\circ + \phi) + \cos (30^\circ - \phi)] \\ &= V_L I_L \cdot 2 \cdot \frac{\sqrt{3}}{2} \cos \phi \\ \therefore W &= \sqrt{3} V_L I_L \cos \phi \end{aligned}$$

Hence, Proved.

10. With necessary phasor diagrams, Prove that,
 (a) In star connected system $V_L = \sqrt{3} V_P$
 (b) In delta connected system $I_L = \sqrt{3} I_P$

Soln:-

(a) In Star connected system,

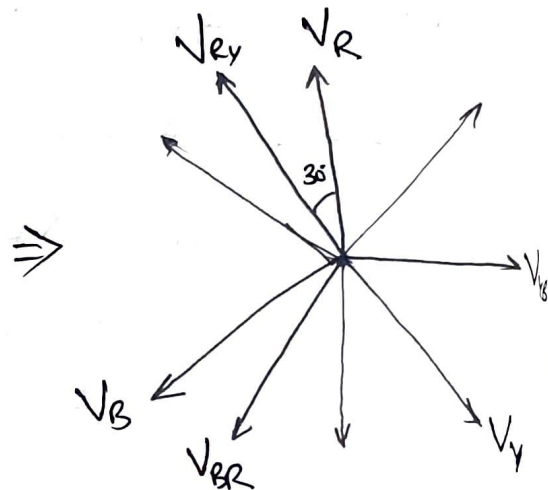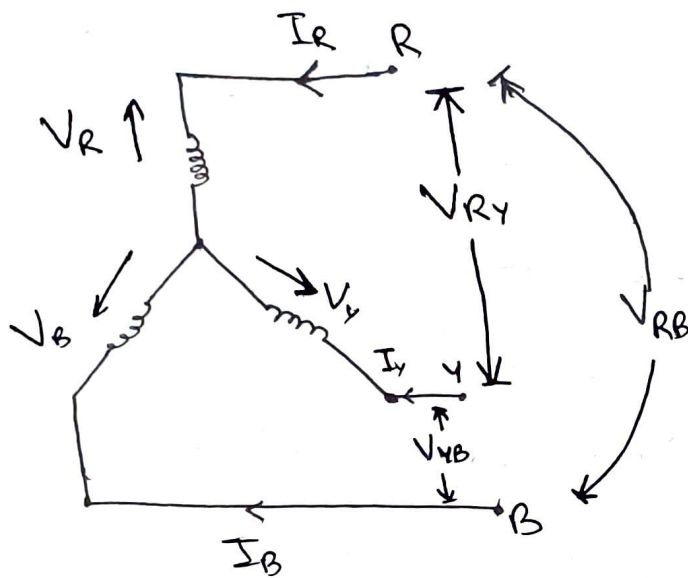

We know,

$$V_R = V_Y = V_B = V_{Ph}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

$$\begin{aligned} \therefore V_{RY} &= V_R - V_Y = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 30^\circ} \\ &= \sqrt{2V_{Ph}^2 + V_{Ph}^2} \end{aligned}$$

$$\therefore V_{RY} = \sqrt{3} V_{Ph}$$


Similarly, $V_{YB} = \sqrt{3} V_{Ph}$

and, $V_{BR} = \sqrt{3} V_{Ph}$

$$\therefore V_L = \sqrt{3} V_P$$

Hence Proved.

(b) In delta connected system,

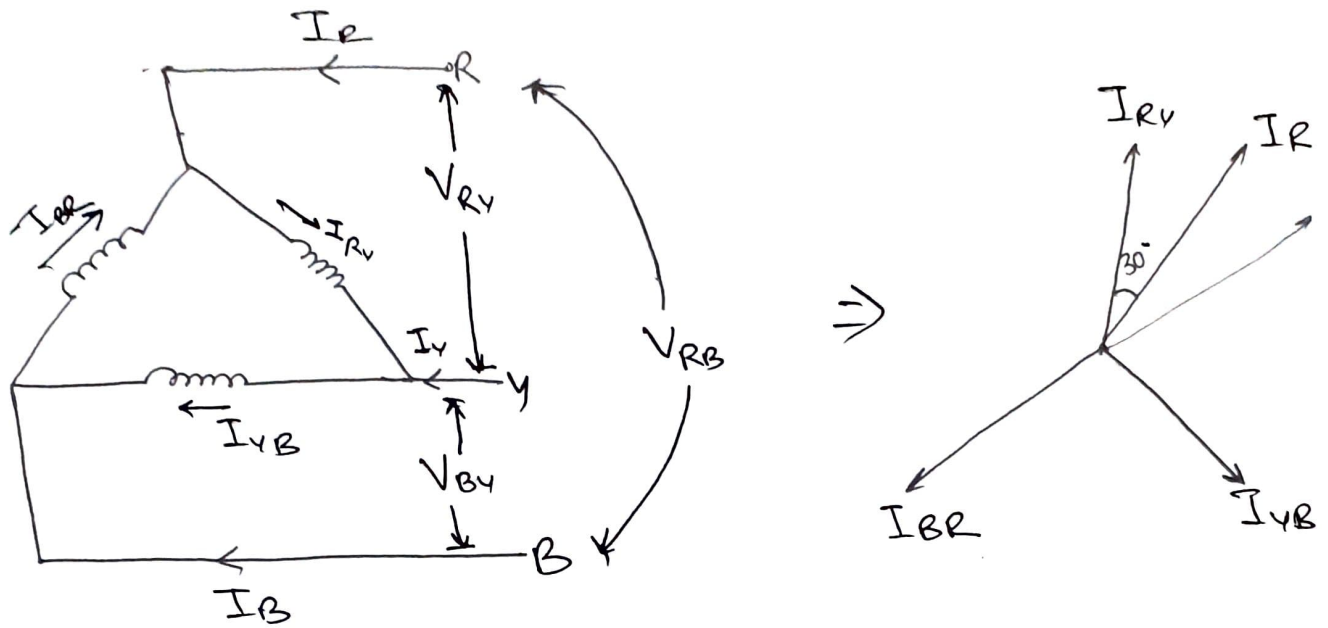

We know,

$$I_R = I_Y = I_B = I_L$$

$$I_{RY} = I_{YB} = I_{BR} = I_{Ph}$$

By KCL, $I_R + I_{BR} = I_{RY}$

$$\begin{aligned} \therefore I_R &= I_{RY} - I_{BR} \\ &= \sqrt{I_{RY}^2 + I_{BR}^2 + 2I_{RY} I_{BR} \cos 30^\circ} \\ &= \sqrt{2I_{Ph}^2 + I_{Ph}^2} \end{aligned}$$

$$\therefore I_R = \sqrt{3} I_{Ph}$$

Similarly, $I_Y = \sqrt{3} I_{Ph}$
 $I_B = \sqrt{3} I_{Ph}$

$$\therefore I_L = \sqrt{3} I_{Ph} \quad \text{Hence, Proved.}$$