

—/—/—

NATIONAL INSTITUTE OF TECHNOLOGY SILCHAR  
CACHAR, ASSAM

LABORATORY EXERCISE BOOK

B.TECH. III<sup>RD</sup> SEM.

NAME: SUBHOJIT GHIMIRE

SCH. ID.: 1912160

BRANCH: CSE - 'B'

SUBJECT: CIRCUIT AND SWITCHING LAB

CODE : EC-222


## AIM: ANALYSIS AND SYNTHESIS OF MULTI-BIT SEQUENTIAL CIRCUITS USING SHIFT REGISTERS.

### THEORY:

A REGISTER capable of shifting information either to right or left is called a shift register. In a shift register, the flip-flops are connected in such a way that the binary bits are entered into the shift register, shifted from one location to another and finally shifted out. There are different types of shift registers, namely - Serial-In-Serial-Out (SISO), Serial-In-Parallel-Out (SIPO), Parallel-In-Parallel-Out (PIPO) and Parallel-In-Serial-Out (PISO).
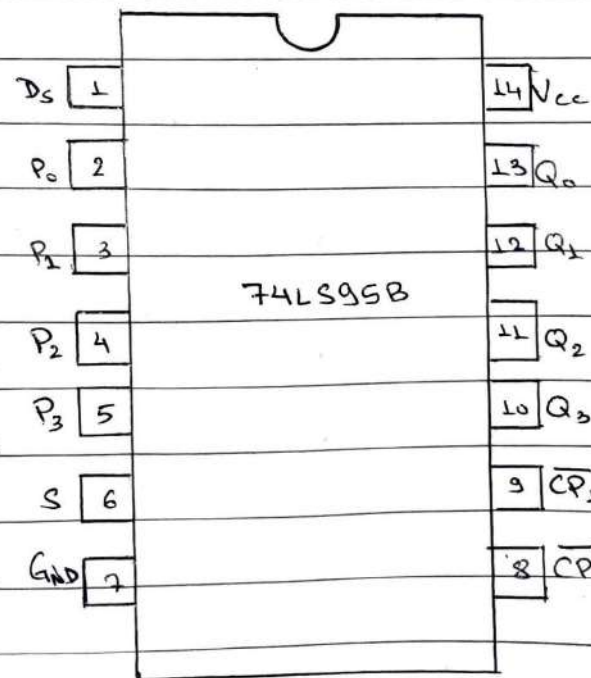
### 4-Bit Shift Register:

The SN54/74LS95B is a 4-bit Shift Register with serial and parallel synchronous operating modes. These operating modes are controlled by a mode control input (S). The serial shift right and parallel load are activated by separate clock inputs which are selected by a mode control input (S). The data is transferred from the serial or parallel D inputs to the Q outputs



synchronous with the HIGH to LOW transition of appropriate clock input.

fig.: 5.1: 74LS95B, 4-bit Shift Register.



\_/\_/\_

PIN NAMES: (as seen in fig 5.1)

$D_s$  : Serial Data Input

$P_0-P_3$  : Parallel Data Inputs

$S$  : Mode Control Input

GND : Ground

$CP_1$  : Serial Clock (Active Low Going Edge) Input

$CP_2$  : Parallel Clock (Active Low Going Edge) Input

$Q_0-Q_3$  : Parallel Outputs

$V_{cc}$  : Voltage Common Collector.

### FUNCTIONAL DESCRIPTION:

The SN54/74LS95B is a 4-bit Shift Register with serial and parallel synchronous operating modes. It has a Serial ( $D_s$ ) and four parallel ( $P_0-P_3$ ) Data inputs, and four parallel ( $Q_0-Q_3$ ) Data Outputs. The serial or parallel mode of operation is controlled by a Mode Control Input ( $S$ ) and two Clock Inputs,  $CP_1$  and  $CP_2$ . When the Mode Control Input ( $S$ ) is HIGH,  $CP_2$  is enabled. A HIGH to Low transition on enabled  $CP_2$  directly loads parallel data from the  $P_0-P_3$  inputs to the  $Q_0-Q_3$  Outputs. When the mode Control Input is Low,  $CP_1$  is enabled. A HIGH to Low transition on an enabled  $CP_1$  transfers the data from Serial Input ( $D_s$ ) to  $Q_0$  and Shifts the data in  $Q_0$  to  $Q_1$ ;  $Q_1$  to  $Q_2$ ;  $Q_2$  to  $Q_3$  respectively (right-shift). For normal operation,  $S$  should only change states when both Clock inputs are LOW. However, changing  $S$  from LOW to HIGH while

\_/\_/\_

CP<sub>2</sub> is HIGH, or changing S from HIGH to LOW while CP<sub>1</sub> is HIGH and CP<sub>2</sub> is LOW will not cause any changes on the register outputs.

OPERATING MODES	INPUTS					OUTPUTS			
	S	CP <sub>1</sub>	CP <sub>2</sub>	D <sub>S</sub>	P <sub>n</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
Shift	L	L	x	L	x	L	q <sub>0</sub>	q <sub>1</sub>	q <sub>2</sub>
	L	L	x	h	x	H	q <sub>0</sub>	q <sub>1</sub>	q <sub>2</sub>
Parallel load	H	x	L	x	P <sub>n</sub>	P <sub>0</sub>	P <sub>1</sub>	P <sub>2</sub>	P <sub>3</sub>

figure 5.2: Truth Table

Here, (on the figure 5.2),

L: is low voltage level

H: is high voltage level

x: is don't care

L: is low voltage one set-up prior to the high to low clock transition

h: is high voltage one set-up prior to the high to low clock transition.

P<sub>n</sub>: is the state of referenced input

 


fig. 5.3: Logic Diagram of 74LS95B

# Circuit Diagram

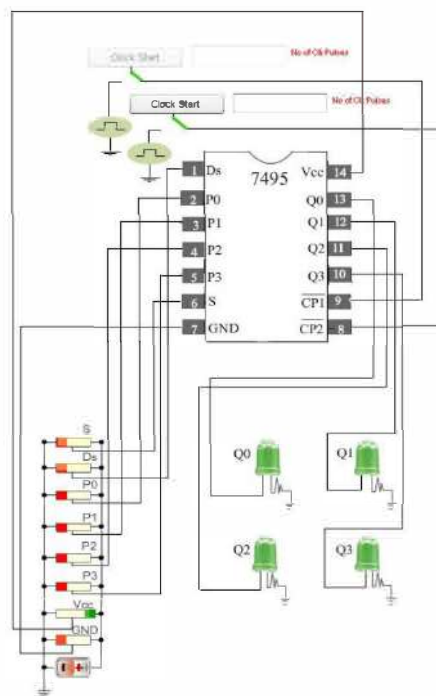


fig. 5.4.: Circuit Diagram of 74LS95B

## Observation

 


fig. 5.5: Timing Diagram of 74LS95B

## RESULT:

The timing diagram was obtained as shown in figure 5.5 after inserting all the inputs. The multi bit sequential circuit was thus ~~successfully~~ successfully analysed and synthesised using shift registers.



**AIM:** TO VERIFY THE TRUTH TABLE AND TIMING DIAGRAM OF 4-BIT SYNCHRONOUS PARALLEL COUNTER AND 4-BIT ASYNCHRONOUS PARALLEL COUNTER BY USING JK FLIPFLOP ICs AND ANALYSE THE CIRCUIT OF 4-BIT SYNCHRONOUS PARALLEL COUNTER AND 4-BIT ASYNCHRONOUS PARALLEL COUNTER WITH THE HELP OF LED'S DISPLAY.

### THEORY:

A counter is a device which stores (and sometimes displays) the number of time a particular event or process has occurred, often in relation to clock signal. Counters are used in digital electronics for counting purpose, they can count specific event happening in the circuit. For example, in UP counter, a counter increases count for every rising edge of clock. Counters are broadly categorised into two - (i) Asynchronous counter. (ii) Synchronous Counter.

#### 1. Asynchronous Counter:

In asynchronous counter, we don't use universal clock, only first flipflop is driven by main clock and the clock inputs of rest of the following counters is driven by output of previous flipflops.

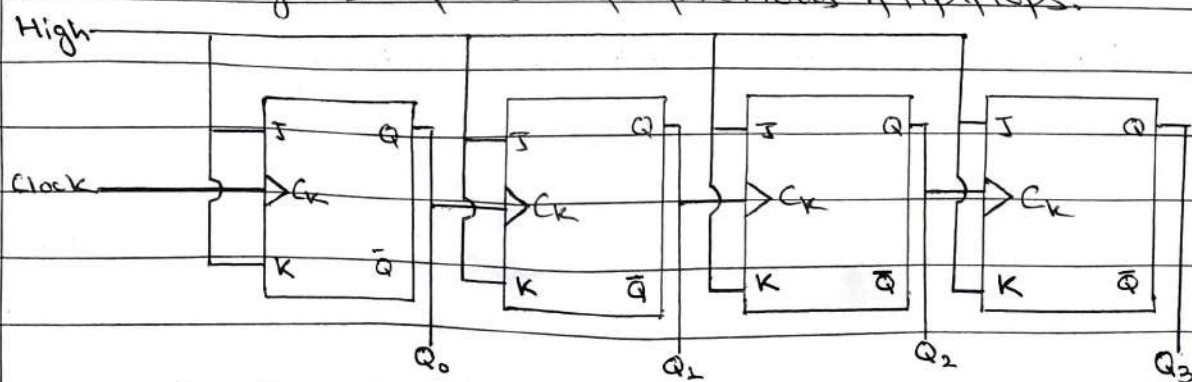


fig. 6.1: Asynchronous Counter Circuit

 


fig. 6.2: Timing Diagram of Asynchronous Counter

It is evident from the timing diagram that  $Q_0$  is changing as soon as the rising edge of clock pulse is encountered;  $Q_1$  is changing when rising edge of  $Q_0$  is encountered (because  $Q_0$  is like clock pulse for second flipflop) and so on. In this way, ripples are generated through  $Q_0$ ,  $Q_1$ ,  $Q_2$  and  $Q_3$ , and hence this counter is also called **RIPPLE counter**.

## 2. Synchronous Counter:

Unlike the asynchronous counter, the synchronous counter has one global clock which drives each flipflop so output changes in parallel. The one advantage of synchronous over asynchronous counter is that it can operate on higher frequency than asynchronous counter as it does not have cumulative delay because of the same clock given to each flipflop.

 


fig. 6.3: Synchronous Counter Circuit.

 


fig. 6.4: Timing Diagram of Synchronous Counter

From the timing diagrams above, we see that  $Q_0$  bit gives response to each falling edge of clock while  $Q_1$  is dependent on  $Q_0$ ;  $Q_2$  is dependent on  $Q_1$  and  $Q_0$ , and finally  $Q_3$  is dependent of  $Q_2$ ,  $Q_1$  and  $Q_0$ .



Circuit Diagram

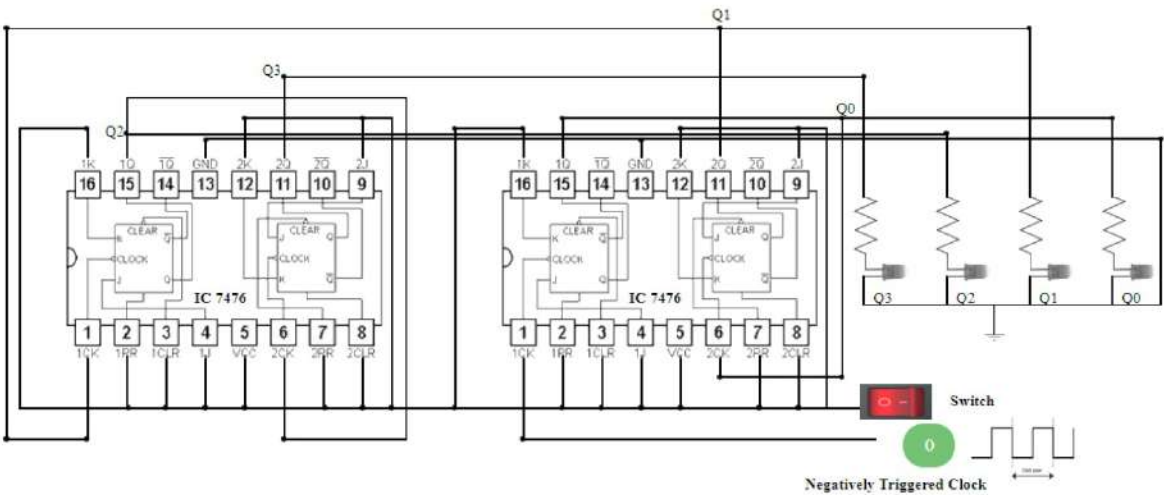


fig. 6.5: 4-Bit Asynchronous Parallel Counter using J-K Flip-Flop

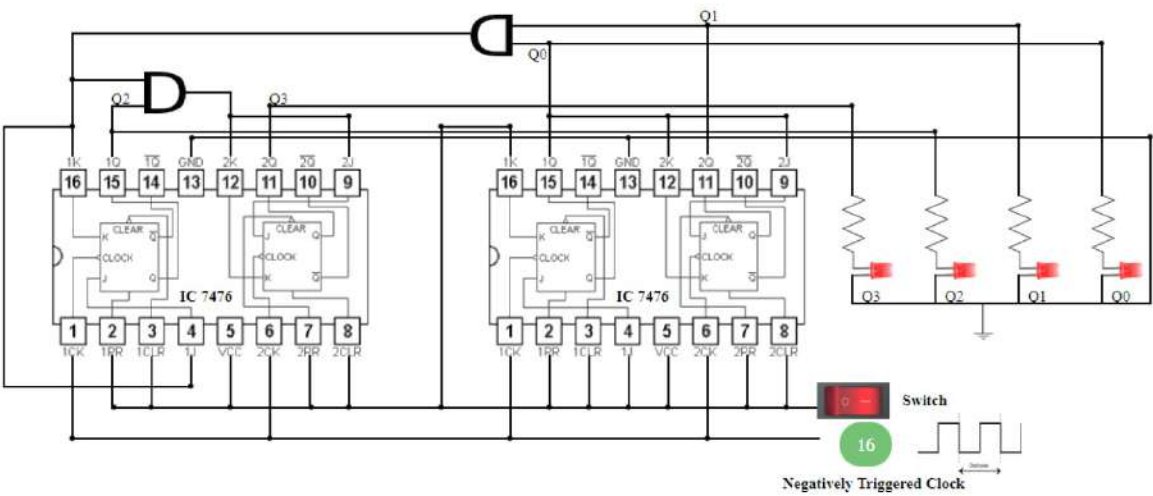


fig. 6.6: Bit Synchronous Parallel Counter using J-K Flip-Flop

# OBSERVATIONS:

Serial No	Clock	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	0	x	x	x	x
2	1	0	0	0	0
3	2	0	0	0	1
4	3	0	0	1	0
5	4	0	0	1	1
6	5	0	1	0	0
7	6	0	1	0	1
8	7	0	1	1	0
9	8	0	1	1	1
10	9	1	0	0	0
11	10	1	0	0	1
12	11	1	0	1	0
13	12	1	0	1	1
14	13	1	1	0	0
15	14	1	1	0	1
16	15	1	1	1	0
17	16	1	1	1	1

Table: 6.1 : Asynchronous Parallel Counter  
Truth Table

# OBSERVATIONS:

Serial No	Clock	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	0	x	x	x	x
2	1	0	0	0	0
3	2	0	0	0	1
4	3	0	0	1	0
5	4	0	0	1	1
6	5	0	1	0	0
7	6	0	1	0	1
8	7	0	1	1	0
9	8	0	1	1	1
10	9	1	0	0	0
11	10	1	0	0	1
12	11	1	0	1	0
13	12	1	0	1	1
14	13	1	1	0	0
15	14	1	1	0	1
16	15	1	1	1	0
17	16	1	1	1	1

Table 6.2: Synchronous Parallel Counter Truth Table



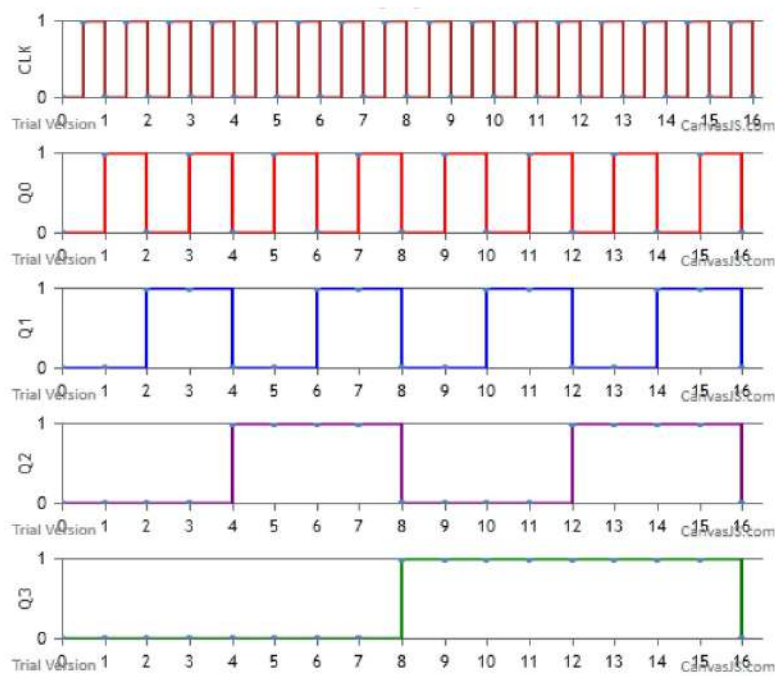


fig. 6.7: Time Diagram of Asynchronous Parallel Counter

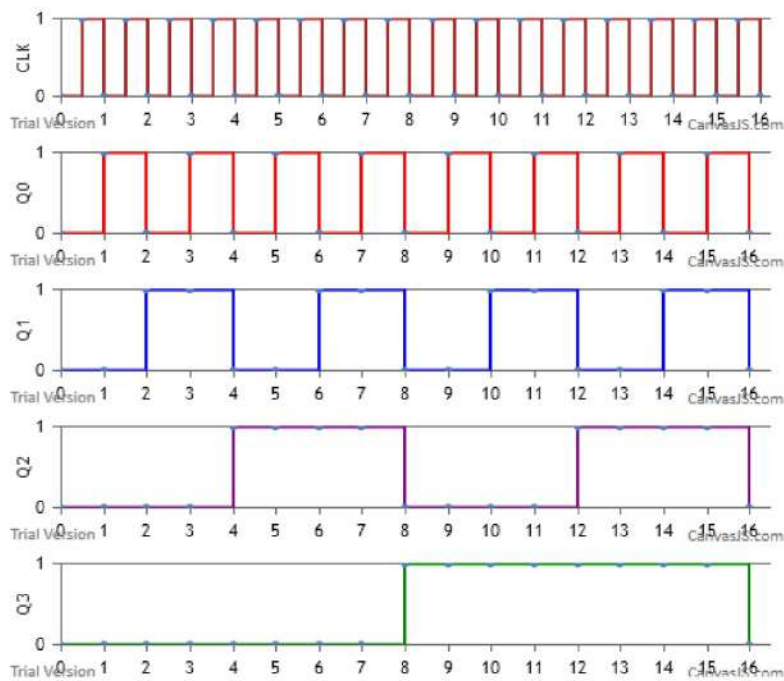


fig. 6.8: Time Diagram of Synchronous Parallel Counter

RESULT:

The truth table for Asynchronous Parallel Counter and its timing diagram were obtained as shown in the table 6.1 and fig. 6.7, respectively. And the truth table and the timing diagram for Synchronous Parallel Counter were obtained as shown in the table 6.2 and fig. 6.8, respectively.