

Name: Subhojit Ghimire

Scholar Id: 1912160

Subject: Electronics Circuit and Switching

Subject Code: EC-221

Semester: III<sup>rd</sup>

Date: 15<sup>th</sup> October, 2020

UG Mid Sem Examination 2020

Branch: CSE

Q.1.

Ans:

	0	1	2					8	9					15	17			21			24
(0, 1, 8, 9)	x	x						x	x												
(1, 9, 17, 25)		x							x						x						
(8, 9, 24, 25)								x	x												x
(0, 2)	x		x																		
(17, 21)															x			x			
(25, 27)																					
(15, 31)														x							
(27, 31)																					

	25		27				31	EQUATION
(0, 1, 8, 9)								$\bar{A}\bar{C}\bar{D}$
(1, 9, 17, 25)	x							
(8, 9, 24, 25)	x							$B\bar{C}\bar{D}$
(0, 2)								$\bar{A}\bar{B}\bar{C}\bar{E}$
(17, 21)								$A\bar{B}\bar{D}E$
(25, 29)	x		x					$AB\bar{C}E$
(15, 31)							x	$BCDE$
(27, 31)			x				x	

∴ The minimised expression is,

$$f = A'B'C'E' + A'C'D' + BC'D' + BCDE + AB'D'E + ABC'E$$

Q.20

Ans)

x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

K-map for input:

x \ yz	00	01	11	10
0			1	
1		1	1	1

$$\therefore A = xy + xz + yz$$


K-map for input:

x \ yz	00	01	11	10
0		1		1
1	1		1	

$$\therefore B = x \oplus y \oplus z$$


$$\therefore C = z'$$

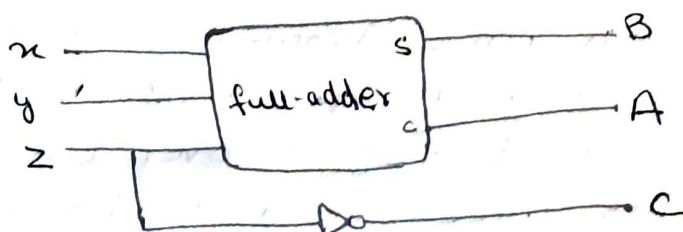The combinational circuit for this would be as follows:




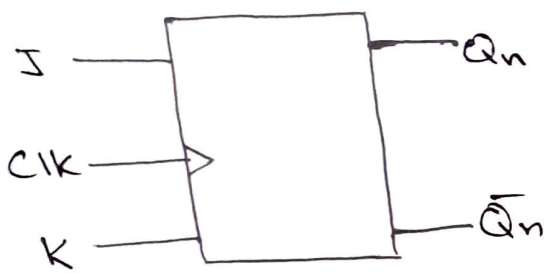Q.3.

Ans: In JK flipflop, the toggling output or the uncontrolled changing, also called the racing condition is triggered when its output compliments or changes from 1 to 0 and 0 to 1. This only happens when the clock is high.




JK level triggered

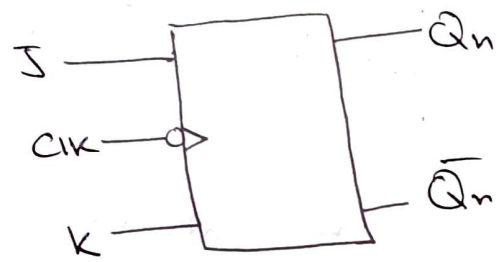

JK edge triggered.

Master Slave Operation of JK flipflop.

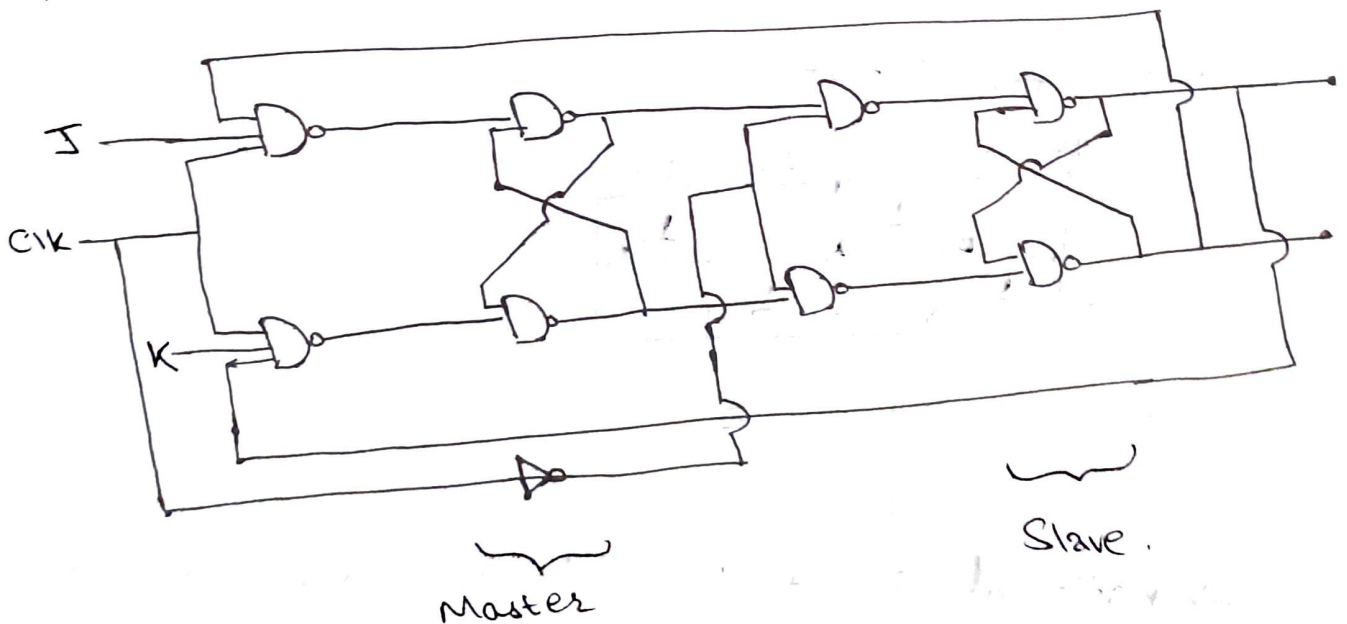

Master

Slave.

- Steps to avoid race around condition:
- (i) Using edge triggering instead of level triggering.
  - (ii) Master Slave circuit toggles over one clock period, which avoids race around condition.

Q.40

Ans

State - Next State table.

Present state			Next State			Next State Decoder		
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$T_2$	$T_1$	$T_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	0	0	0	1	1	0
1	1	1	X	X	X	X	X	X

$$T_0 = \overline{Q_2} + \overline{Q_0}$$

$$T_1 = Q_1 + Q_0 Q_2$$

$$T_2 = Q_2 Q_1 + Q_0 Q_2$$


$Q_2 Q_1$	00	01	11	10
0	1	1	1	1
1	1	1	X	0

for  $T_0$ 

$Q_2 Q_1$	00	01	11	10
0	0	1	1	0
1	0	1	X	1

for  $T_1$ 

$Q_2 Q_1$	00	01	11	10
0	0	0	1	0
1	0	0	X	1

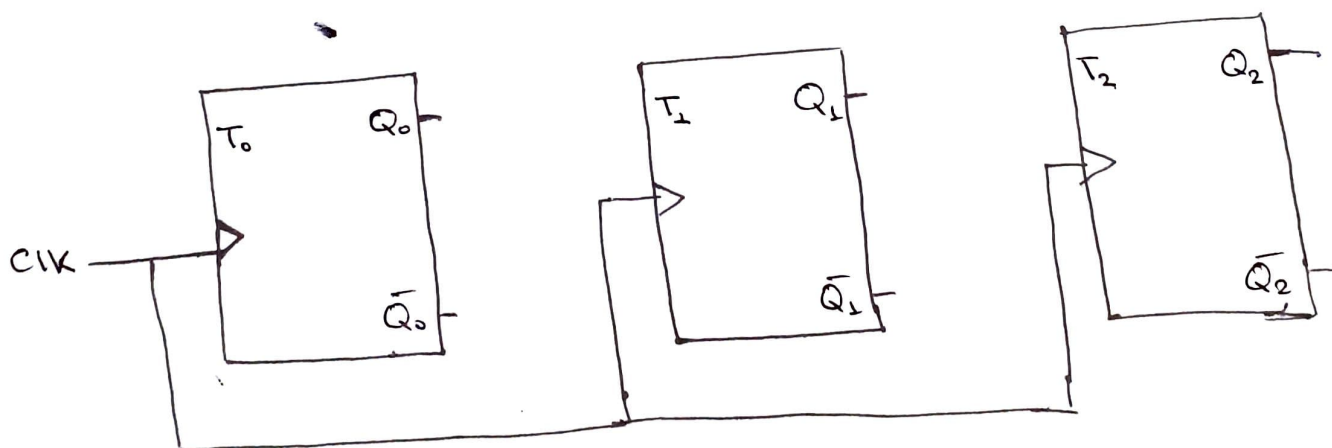for  $T_2$  $\overline{Q_2}$  $Q_0$  $Q_1$  $\overline{Q_0}$