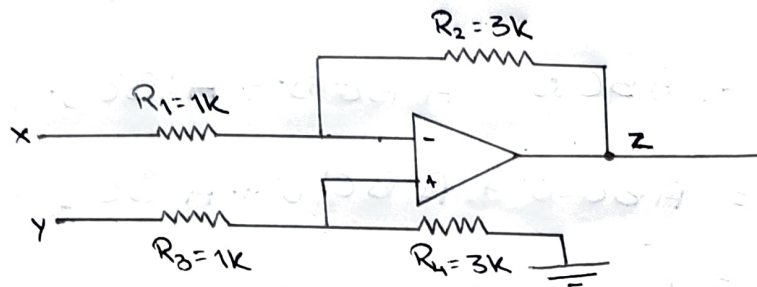


Q.1. Find the output voltage at node Z.



Soln: When $y = 0$,
for inverting amplifier circuit,

$$Z_1 = -\frac{R_2}{R_1} \cdot x$$

$$\therefore Z_1 = -3x$$

When $x = 0$,

$$y_0 = \frac{y R_4}{R_4 + R_3} = \frac{3y}{4}$$

And, for non-inverting amplifier circuit

$$Z_2 = \left(1 + \frac{R_2}{R_3}\right) y_0$$

$$= 4 \cdot \frac{3y}{4}$$

$$\therefore Z_2 = 3y$$

Hence,

$$Z = Z_1 + Z_2$$

$$\therefore Z = -3x + 3y$$

$$\therefore Z = 3y - 3x$$


Q.2. Implement the following boolean expression using a 4:1 multiplexer?

$$F = ABC'D' + A'BC'D' + A'BCD' + ABC'D$$

Soln:

$$\begin{aligned} F &= ABC'D' + A'BC'D' + A'BCD' + ABC'D \\ &= A(BC'D' + BC'D) + A'(BC'D' + BCD') \\ &= AB(C'(D' + D)) + A'BD'(C' + C) \\ &= ABC' + A'BD' \end{aligned}$$

So, in multiplexer:

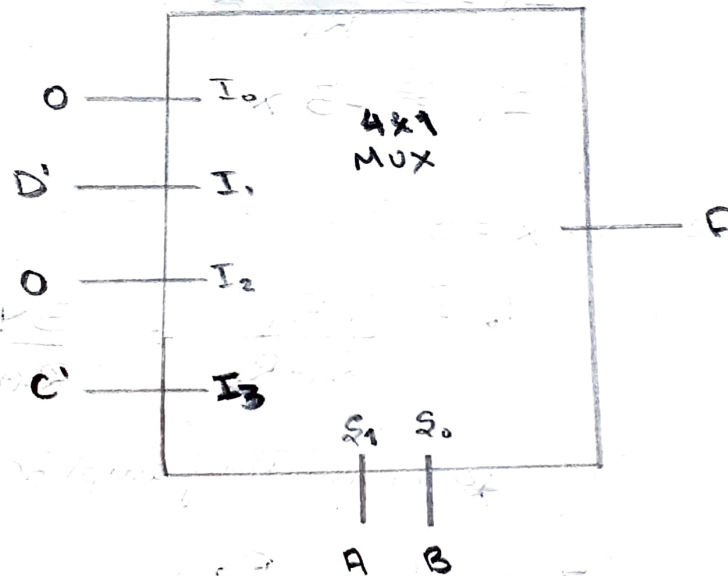


Q.3. Implement XOR gate function with 2:1 MUX.


Soln:

$$F = A'B + AB' = A \oplus B$$

So, in multiplexer,

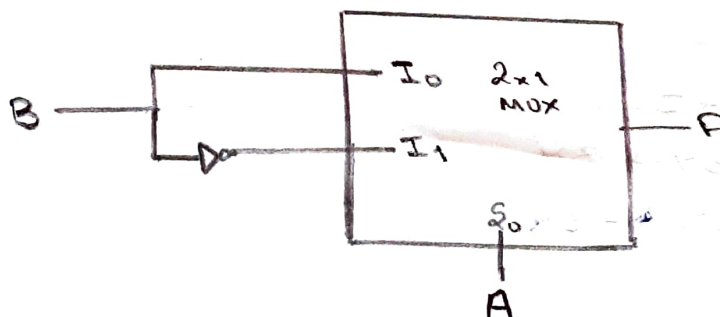

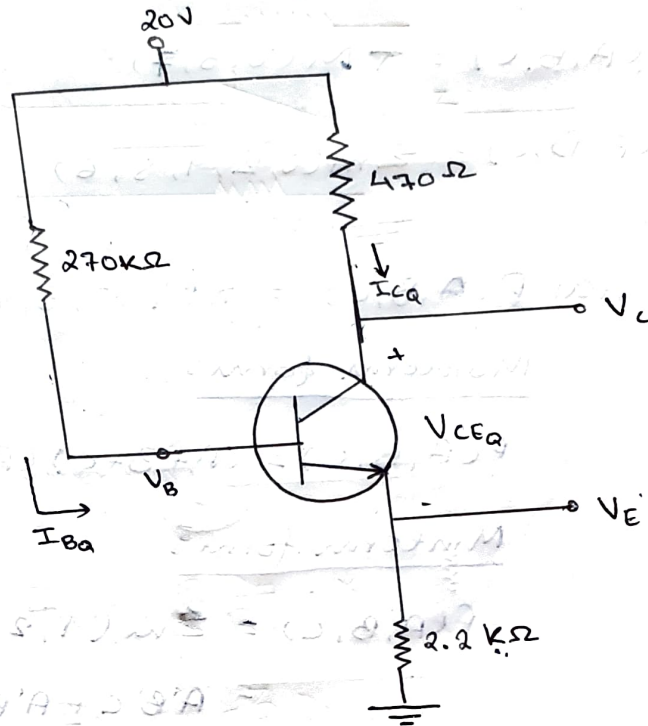Q.4. For the emitter-bias configuration given below, determine I_{BQ} , I_{CQ} , V_{CEQ} , V_C , V_B and V_E .



Soln:- from KVL,

$$20 = 270 I_{BQ} + V_{BE} + 2.2 I_{EQ}$$

$$\text{a, } 20 = 270 I_{BQ} + 0.7 + 2.2 (1 + \beta) I_{BQ}$$

$$\text{a, } 20 - 0.7 = I_{BQ} (270 + (1 + 125) 2.2)$$

$$\therefore I_{BQ} = 0.035 \text{ mA}$$

$$\text{So, } I_{EQ} = (1 + \beta) I_{BQ} = 126 \times 0.035 = 4.41 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 125 \times 0.035 = 4.37 \text{ mA}$$

Again from KVL,

$$20 = I_{CQ} \times \frac{470}{1000} + V_{CEQ} + I_{EQ} \times 2.2$$

$$\therefore V_{CEQ} = 8.238 \text{ V}$$

So,

$$V_{BE} = V_B - I_{EQ} R_E$$

$$\text{a, } V_B = 0.7 + 4.41 \times 2.2$$

$$\therefore V_B = 10.402 \text{ V}$$

Q.5. Express the following Boolean Algebraic functions in maxterms and minterms.

(a) $F(A, B, C) = \pi M(0, 3, 7)$

(b) $F(A, B, C) = \sum m(0, 2, 4, 5, 6)$

Soln:-

(a) $F(A, B, C) = \pi M(0, 3, 7)$

Maxterm form:

$$F(A, B, C) = (A+B+C)(A+B'+C')(A'+B'+C)$$

Minterm form:

$$F(A, B, C) = \sum m(1, 2, 4, 5, 6)$$

$$= A'B'C + A'BC' + AB'C' + AB'C + ABC'$$

(b) $F(A, B, C) = \sum m(0, 2, 4, 5, 6)$

Minterm form




$$F(A, B, C) = A'B'C' + A'BC' + AB'C' + AB'C + ABC'$$

Maxterm form


$$F(A, B, C) = \pi M(1, 3, 7)$$

$$= (A+B+C')(A+B'+C')(A'+B'+C)$$

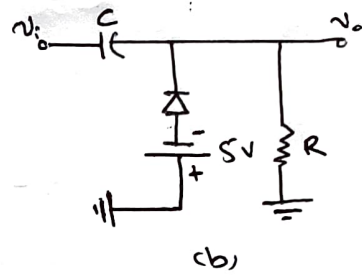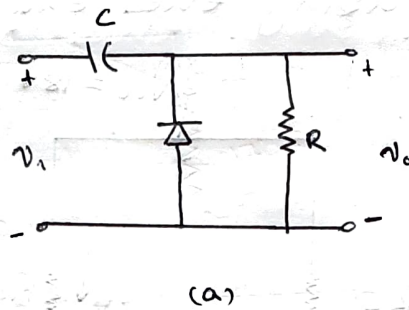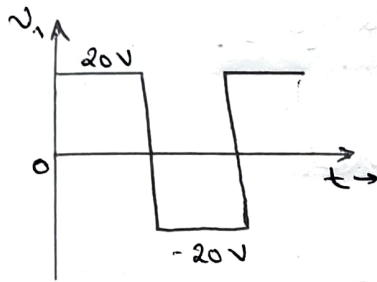Q.6. Determine output voltage and sketch V_o for the network shown in fig. (a) and (b) below:




Soln:- for (a), Output signal waveform:

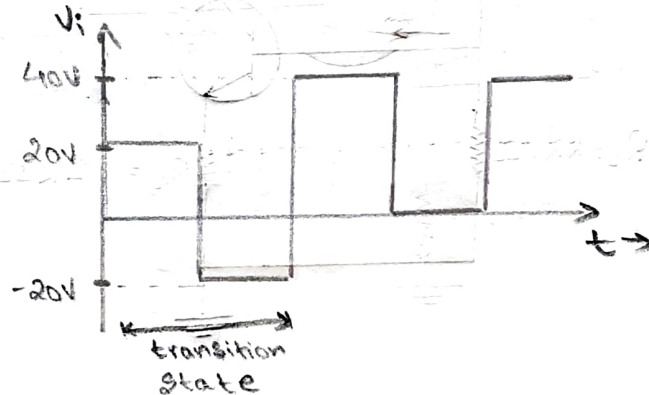


So, Output voltage, $V_o = 40V$

for (b), Output signal waveform:

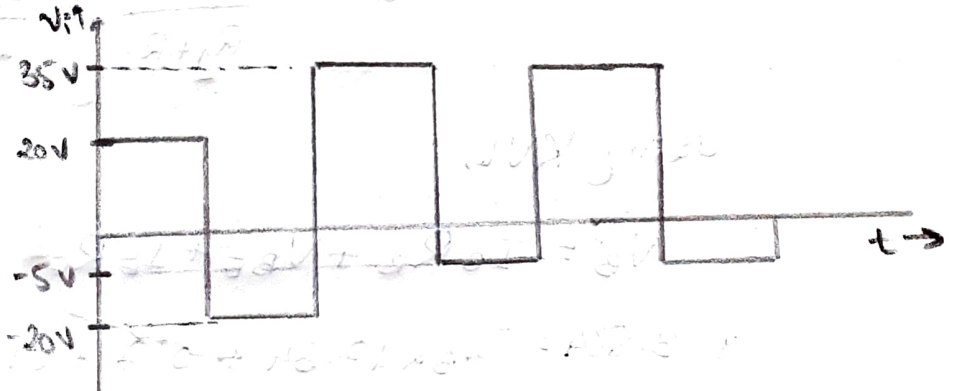

So, Output voltage, $V_o = 35V$

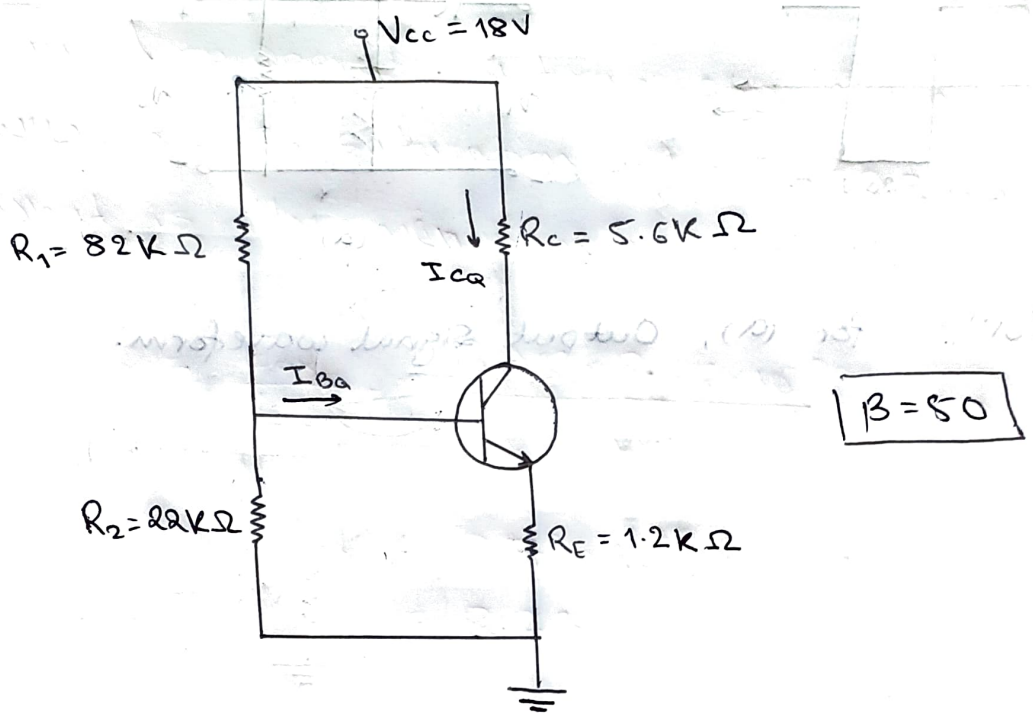Q.7. Determine the levels of I_{CQ} and V_{CEQ} for the voltage-divider configuration for the given circuit using the exact analysis.



Soln:-

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{18 \times 22}{22 + 82} = 3.807\text{V}$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{22 \times 82}{22 + 82} = 17.34\text{k}\Omega$$

Using KVL,

$$V_B = I_B R_B + V_{BE} + I_E R_E$$

$$3.804 = I_B \times 17.34 + 0.7 + (1 + \beta) I_B \times 1.2$$

$$\therefore I_{BQ} = 0.0395\text{mA}$$

$$I_{CQ} = \beta I_{BQ} = 50 \times 0.0395 = 1.977\text{mA}$$

$$I_{EQ} = (1 + \beta) I_{BQ} = 51 \times 0.0395 = 2.01\text{mA}$$

Also, from KVL,

$$V_{CC} = I_{CQ} R_C + V_{CE} + I_{EQ} R_E$$


$$\therefore 18 = 1.977 \times 5.0 + V_{CE} + 2.07 \times 1.2$$

$$\therefore V_{CEQ} = 4.5084 \text{ V}$$

\therefore The required values of I_{CQ} and V_{CEQ} are 1.977 mA and 4.5 V respectively.

Q.8 (a) Using approximate characteristics for the Si diode, determine V_D , I_D and V_R for the circuit of given figure.

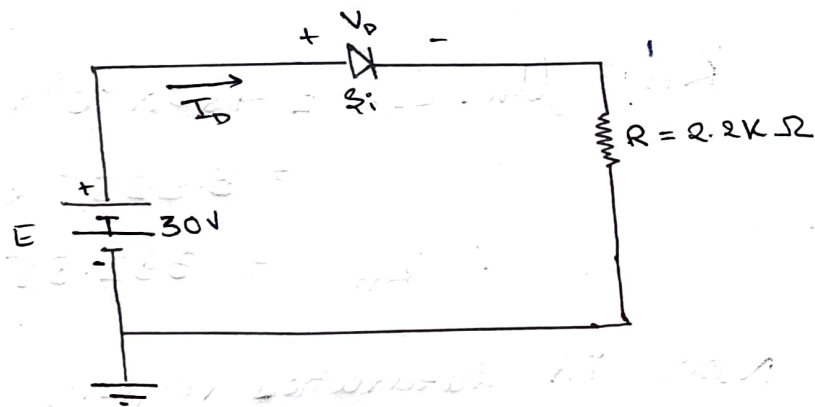(b) Perform the same analysis as part (a) using the ideal model for the diode.



Soln:-

(a) $V_D = 0.7 \text{ V}$ (for Si-diode)

Using KVL,

$$30 = 0.7 + I_D R$$

$$\therefore I_D = 13.31 \text{ mA}$$

(b) $V_D = 0 \text{ V}$ (for ideal diode)

Using KVL,

$$30 = 0 + I_D R$$

$$\therefore I_D = 13.63 \text{ mA}$$

C_{ox} , K'_n and the overdrive voltage V_{ov} required to operate a transistor having

$(W/L) = 20$ in saturation with $I_D = 0.3 \text{ mA}$.

What is the minimum value of V_{DS} needed?

Soln:-

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.95 \times 8.55 \times 10^{-12}}{4 \times 10^{-9}}$$

$$\therefore C_{ox} = 8.73 \times 10^{-3} \text{ F/m}^2$$

$$= 8.73$$

$$K'_n = \mu_n \cdot C_{ox} = 450 \times 10^8 \times 8.73 \times 10^{-15}$$
$$= 3.9285 \times 10^{-4}$$

$$\therefore K'_n = 392.85 \text{ } \mu\text{A/V}^2$$

Now, in saturation region,

$$I_D = \frac{K'_n}{2} \left(\frac{W}{L} \right) \left(\frac{V_{ov}}{1} \right)^2$$

$$\text{Q, } 300 = \frac{392.85}{2} \times 20 \times (V_{ov})^2$$

$$\therefore V_{ov} = 0.27 \text{ V}$$

\therefore Minimum V_{DS} required,

$$V_{DS_{min}} = V_{ov} = 0.27 \text{ V}$$

Q.10. An NMOS transistor is operating at the edge of saturation with an overdrive voltage V_{ov} and a drain current I_D . If V_{ov} is doubled, and we must maintain operation at the edge of saturation, what should V_{DS} be changed to? What value of drain current results?

Soln:-

Initially,

$$I_D = \frac{K_n}{2} V_{ov}^2$$

for saturation region, ($V_{DS} \geq V_{ov}$)

$$\therefore V_{DS} = V_{ov}$$

Finally,

$$V_{ovf} = 2V_{ov}$$

At Saturation region,

$$\begin{aligned} V_{DSf} &= \frac{K_n}{2} (V_{ovf})^2 \\ &= \frac{K_n}{2} (2V_{ov})^2 \end{aligned}$$

$$\therefore V_{DSf} = 4I_D$$

So, the current will increase by 4 times.